

ISL6420B

Design Calculations

for the

FireMC-PiHat (FireMC-3.14)

Required references:

Intersil ISL6420B Datasheet < <http://www.intersil.com/en/products/power-management/switching-controllers/single-output---buck-controllers/ISL6420B.html> >

ST Microelectronics STD86N3LH5 Datasheet <http://www.st.com/content/st_com/en/products/power-transistors/power-mosfets/n-channel-stripfet-12-v-to-30-v/std86n3lh5.html>

Schelle, D., et al: (2006, June). Buck-Converter Design Demystified. *Power Electronics Technology*. Retrieved from <http://powerelectronics.com/dc-dc-converters/buck-converter-design-demystified>

ISL 6420 B DESIGN CALCULATIONS

FIREML-3.14

PAGE 1

$$V_{IN(MIN)} = 11V \quad f_{sw} = 300000$$

$$V_{IN(NOM)} = 12V \quad LIR = 0.3$$

$$V_{IN(MAX)} = 13V \quad I_{OUT(MAX)} = 4A$$

$$V_{OUT} = 3V3$$

$$L = \frac{(V_{IN(MAX)} - V_{OUT}) V_{OUT}}{V_{IN(MAX)} f_{sw} LIR I_{OUT(MAX)}} \\ = 6.84 \mu H \quad \text{CHOOSE} \quad 6.8 \mu H$$

$$\Delta I_L = LIR (I_{OUT(MAX)}) = \frac{(V_{IN(MAX)} - V_{OUT}) V_{OUT}}{V_{IN(MAX)} f_{sw} L} \\ \approx 1.2 A$$

$$I_{OUT(PK)} = I_{OUT(MAX)} + \frac{\Delta I_L}{2} \\ = 4 + 1.2 \\ = 5.2 A \quad \text{CHOOSE } I_{L(SAT)} > I_{OUT(PK)} (1.2) = 6.26 A$$

$$\Delta I_L (ACT) = \frac{(V_{IN(MAX)} - V_{OUT}) V_{OUT}}{V_{IN(MAX)} f_{sw} L} \\ = 1.21 A$$

$$C_0 = L \left(I_{OUT(MAX)} + \frac{\Delta I_L (ACT)}{2} \right)^2 \quad \Delta V = 0.1 V \\ \frac{(\Delta V + V_{OUT})^2 - V_{OUT}^2}{} \\ = 275 \mu F$$

$$C_0 (ACT) = C_0 + 20\% \\ = 331 \mu F \quad \text{CHOOSE } 470 \mu F$$

$$V_{OUT(CAP)} = \frac{V_{IN(MAX)} - V_{OUT}}{2 C_O L} \left(\frac{V_{OUT}}{V_{IN(MAX)} f_{SW}} \right)^2$$

$$=$$

$$V_{OUT(ESR)} = \Delta I_L (ESR_{CO})$$

$$V_{OUT(RIPPLE)} = 2\% = 0.066V$$

$$ESR_{CO} = \frac{1}{\Delta I_L} \left(V_{OUT(RIPPLE)} - \frac{V_{IN(MAX)} - V_{OUT}}{2 C_O L} \left(\frac{V_{OUT}}{V_{IN(MAX)} f_{SW}} \right)^2 \right)$$

$$= 0.0537 \Omega$$

$$I_{CIRMS} = I_{OUT(MAX)} \frac{\sqrt{V_{OUT}(V_{IN} - V_{OUT})}}{V_{IN}}$$

$$= 1.79A$$

$$C_I = \frac{10\mu F (I_{CIRMS})}{1A} \text{ TO } \frac{22\mu F (I_{CIRMS})}{A}$$

$$= 17.9\mu F \text{ TO } 39.4\mu F$$

CHOOSE $20\mu F$ TO $40\mu F$

$$T_{J(MAX)} = 115^\circ C$$

$$T_{A(MAX)} = 60^\circ C$$

$$T_{J(RISE)} = T_{J(MAX)} - T_{A(MAX)}$$

$$= 55^\circ C$$

$$P_{D(TOT)} = \frac{T_{J(RISE)}}{\Theta_{JA}}$$

$$\Theta_{JA} = 52^{\circ}\text{C/W}$$

$$= 1.06 \text{ W}$$

$$R_{DS(ON)[HOT]} = [1 + 0.005 (T_{JHOT} - 25^{\circ})] R_{DS(ON)25}$$

$$R_{DS(ON)25} = \left(\frac{V_{IN(MIN)}}{V_{OUT}} \right) \left(\frac{1}{I_{OUT(MAX)}^2 [1 + 0.005 (T_{JHOT} - 25^{\circ})]} \right) (P_{TOT} / 0.6)$$

$$R_{DS(ON)25} \leq 0.091 \Omega$$

$$\text{STD86N3LH5 } R_{DS(ON)25} \leq 0.065 \Omega$$

** ESTIMATE (REQUIRES LAB VERIFICATION) **

$$P_{D(SW)} = \frac{C_{RSS} (V_{IN(MAX)})^2 (f_{SW}) (I_{OUT(MAX)})}{I_{GATE}}$$

$$C_{RSS} = 38 \text{ pF}$$

$$I_{GATE} = 0.7 \text{ A}$$

$$= 0.0168 \text{ W}$$

** END ESTIMATE **

$$R_{DS(ON)[HOT]} = 0.09425 \Omega$$

$$P_{D(RDS)} = \frac{V_{OUT} I_{OUT(MAX)}^2 R_{DS(ON)[HOT]}}{V_{IN(MIN)}}$$

$$= 0.45264 \text{ W}$$

$$P_D = P_{D(RDS)} + P_{D(SW)}$$

$$T_{J(RISE)[EST]} = P_D (\Theta_{JA})$$

$$= 0.547 \text{ W}$$

$$= 28.44$$

$$T_J = 88.44^{\circ}$$

$$I_{OC} > I_{OUT(PK)} + 20\%$$

$$I_{OC} \geq 6.26A$$

$$I_{OC} = \frac{I_{OCSET} R_{OCSET}}{R_{DS(ON)(MAX)}}$$

$$R_{DS(ON)90} \approx 1.375 R_{DS(ON)25}$$

$$\approx 0.090 \Omega$$

$$R_{DS(ON)90} = R_{DS(ON)MAX}$$

$$R_{OCSET} = \frac{I_{OC} (R_{DS(ON)MAX})}{I_{OCSET}}$$

$$= 5670 \Omega \quad \text{CHOOSE } 5.76k\Omega$$

* SEE FIGURE 17 SHEET 17 OF ISL6420B DATASHEET FOR THE BELOW

$$f_{LL} = \frac{1}{2\pi \sqrt{L(C_0)}}$$

$$= 2877 Hz$$

$$f_{ESR} = \frac{1}{2\pi (ESR_{CO} C_0)}$$

$$ESR_{CO(FACT)} = 0.05333$$

$$= 6632 Hz$$

$$V_1 = \frac{V_2 R_H}{R_I + R_H}$$

$$V_2 = V_{OUT}$$

$$V_1 = 0.594 - 0.606$$

$$R4 = \frac{V1 R1}{V2 - V1}$$

$$R4 = \frac{0.594 (10000)}{3.3 - 0.594}$$

$$= 2195 \Omega$$

$$R4 = \frac{0.606 (10000)}{3.3 - 0.606}$$

$$= 2250$$

CHOOSE $R4 = 2.21k$
 $R1 = 10k$

$$R2/R1 = 5.62$$

$$R2 = 56.2k$$

$$f_{z1} = 0.75 f_{LC} = \frac{1}{2\pi R2 C1}$$

$$C1 = \frac{1}{2\pi R2 0.75 f_{LC}}$$

$$= 1.66 nF \quad \text{CHOOSE } 1600pF$$

$$f_{z2} = f_{LC} = \frac{1}{2\pi (R1 + R3) C3}$$

$$\frac{f_{sw}}{2} = \frac{1}{2\pi R3 C3}$$

$$f_{LC} = \frac{1}{2\pi \left(R1 + \frac{1}{2\pi (f_{sw}/2) C3} \right) C3}$$

$$R3 = \frac{1}{2\pi (f_{sw}/2) C3}$$

$$C3 = \frac{f_{sw}/2}{f_{LC}} - 1$$

$$\frac{2\pi R1 (f_{sw}/2)}{}$$

$$= 6.88 \text{ nF} \quad \text{CHOOSE} \quad 6800 \text{ pF}$$

$$R3 = \frac{1}{2\pi (f_{sw}/2) C3}$$

$$= 156 \quad \text{CHOOSE} \quad 158 \Omega$$

$$f_{p1} = \frac{1}{2\pi (R2) \left(\frac{C1 C2}{C1 + C2} \right)} = f_{ESR}$$

$$\frac{C1 C2}{C1 + C2} = \frac{1}{2\pi (R2) (f_{p1})}$$

$$C1 C2 = \frac{C1 + C2}{2\pi (R2) (f_{ESR})}$$

$$C2 = \frac{C1}{2\pi f_{ESR} (R2) (C1) - \left(\frac{1}{2\pi} \right)}$$

$$= 582.46 \text{ pF} \quad \text{CHOOSE} \quad 560 \text{ pF}$$